 


### Design Exercise 3 OTA

An Operational Transconductance Amplifier (OTA) is a voltage-controlled current source (VCCS) that converts an input differential voltage into an output current.

The circuit shown represents a two-stage CMOS OTA:



The structure of this OTA includes two amplification stages, a biasing circuit, and a compensation network, all working together to achieve robust performance.

The first stage of the OTA is a differential amplifier composed of transistors M1 and M2, forming the input pair, with M3 and M4 serving as active loads implemented as a current mirror. This configuration ensures a high input impedance, making the circuit ideal for interfacing with high-impedance sources while providing the initial voltage gain. Furthermore, the tail current source, implemented with M6, stabilizes the bias current for the input transistors, ensuring precise operation over varying conditions.

The second stage of the OTA provides additional voltage gain through transistor M5, which amplifies the signal from the first stage. The current mirror composed of M7 and M8 in the second stage ensures proper current steering and further contributes to the circuit's efficiency.

This design achieves high gain through the combined contributions of the two amplification stages, which can be expressed approximately as:

$$A_v = g_{m1,2} \cdot g_{m5} \cdot (r_{o3} || r_{o1,2}) \cdot r_{o5}$$


In this circuit, compensation is achieved using the Miller capacitor  $C_c$  and, optionally, a series resistor  $R_c$ . The Miller capacitor introduces a dominant pole at the output of the first stage, effectively reducing the gain at higher frequencies.

The addition of the optional resistor  $R_c$  in series with  $C_c$  can further improve the phase margin. This is achieved by introducing a low-frequency zero that cancels out one of the non-dominant poles, thereby reducing the phase lag caused by higher-frequency poles. The result is a more stable amplifier with improved transient response and a wider range of stable feedback conditions.

The design specifications are:

Parameter	Value	Physical
VDD	1	<i>Volts</i>
VSS	-1	<i>Volts</i>
Minimum small signal Gain - $A_0$	60	<i>dB</i>
Minimum GBW	100	<i>MHz</i>
Load Capacitance	10	<i>pF</i>
Phase Margin	>45	<i>Degrees</i>
Power Dissipation	Keep as low as possible	<i>Watts</i>
Dynamic range	Keep as high as possible	



## Circuit Schematic

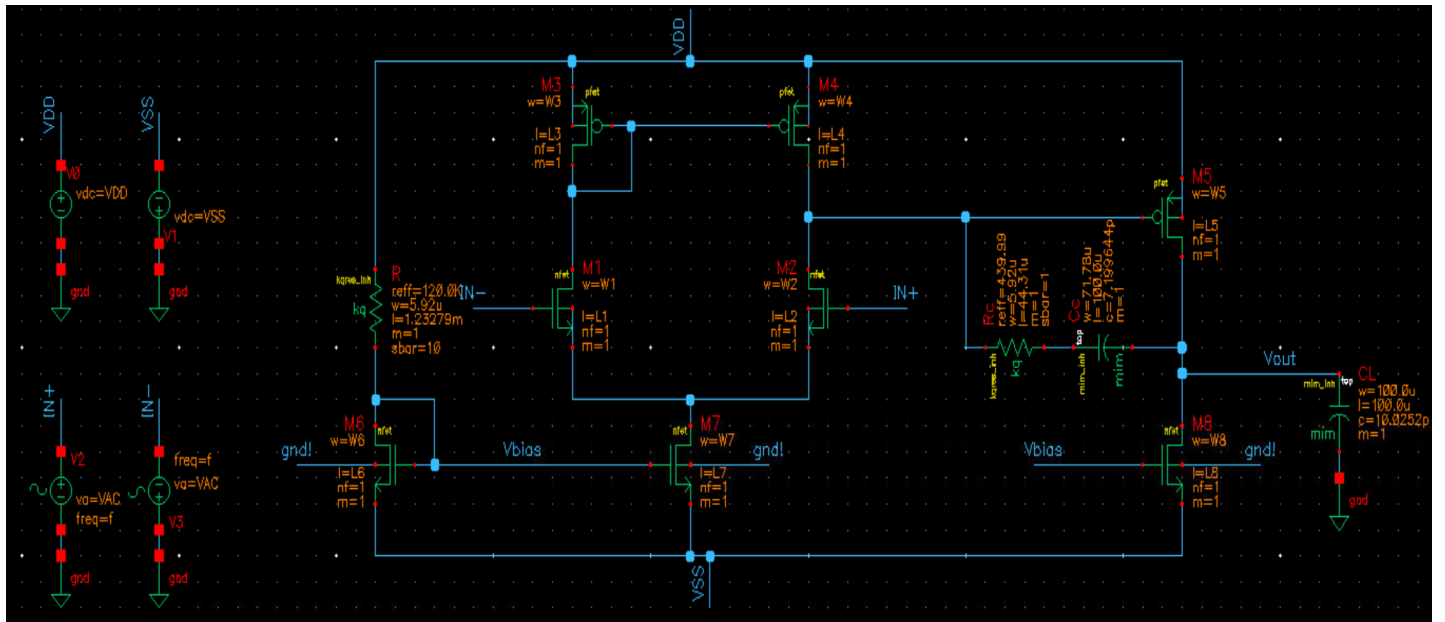


## Device Dimensions table

	Total width ( $\mu\text{m}$ )	Length ( $\mu\text{m}$ )	$g_m$ ( $\Omega^{-1}$ )	$g_{ds}$ ( $\Omega^{-1}$ )	Resistance ( $\Omega$ )	Capacitance (pF)
$M_1$	56	0.5	2.745m	41.4u		
$M_2$	56	0.5	2.745m	41.4u		
$M_3$	34	0.5	1.056m	50.27u		
$M_4$	34	0.5	1.056m	50.27u		
$M_5$	155	0.5	5.409m	132.1u		
$M_6$	7	0.5	479.3u	1.002m		
$M_7$	35	0.5	3.269m	69.75u		
$M_8$	83.5	0.5	8.619m	124.8u		
$R$					120K	
$R_c$					440	
$C_c$						7.2

## Circuit Operation Point

 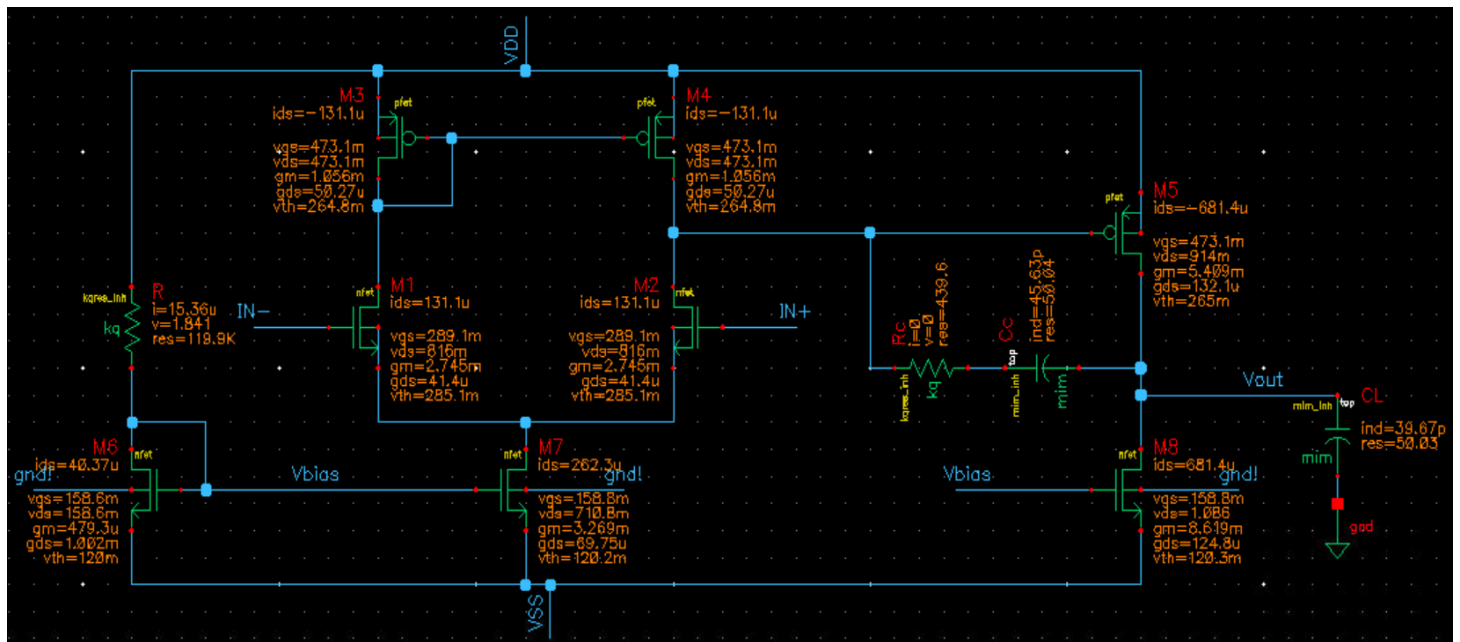

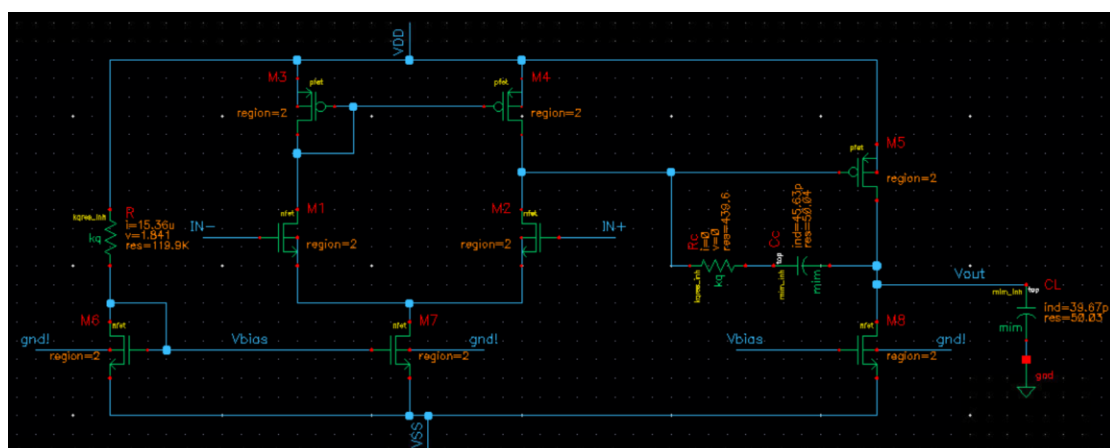All the transistors are in saturation region.



**DC Power Consumption**

The total DC power consumption of the circuit is determined by the currents drawn from the power supplies and their respective voltages.

Using the following standard formula, the total power is calculated by considering the contributions from both the positive  $V_{DD}$  and negative  $V_{SS}$  supply rails:

$$P_{total} = V_{DD} \cdot I_{DD} + |V_{SS}| \cdot I_{SS}$$

The simulation provides an accurate estimation of the circuit's power consumption under DC conditions:


average(getData(":pwr" ?result "tra... x

Expression	Value
average(getData(":pwr" ?result "tran"))	6.063E-3

Window 219

14:17:41 Sun Jan 12 2025

 **Transient Analysis `tran': time = (0 s -> 20 ms)**



## AC Simulation: Gain and Phase response

An AC analysis was conducted to determine the amplifier's frequency response. The results indicate that the amplifier achieves a low-frequency gain of **61.8 dB**, a gain-bandwidth product of **303.26 MHz**, and exhibits the expected phase behavior across the frequency range.


These results confirm that the amplifier's performance aligns with the required metrics.

**Important note:** This simulation was performed without the compensation loop. The effect of using  $R_c$  and  $C_c$  on the gain and phase came later in the "Stability Simulation" section.

OTA\_two\_stage\_3 : OTA two\_stage schematic

20:45:15 Sun Jan 12 2025

### AC Response

 



## AC Simulation: CMRR

The Common-Mode Rejection Ratio (CMRR) quantifies an amplifier's ability to reject signals that appear simultaneously at both inputs, relative to how it amplifies differential signals.

Mathematically, it is the ratio of the differential gain  $A_{diff}$  to the common-mode gain  $A_{cm}$ :


$$CMRR = \frac{A_{diff}}{A_{cm}}$$

Often, we express it in decibels (dB) as:

$$CMRR_{dB} = 20\log_{10}(CMRR) = 20\log_{10}\left(\frac{A_{diff}}{A_{cm}}\right) = 20\log_{10}(A_{diff}) - 20\log_{10}(A_{cm})$$

The calculated CMRR from the simulation was **65.61701 dB**.

 Green -  $A_{diff}$       Pink -  $A_{cm}$       Red - CMRR



### AC Simulation: I/O impedance


The impedance measurements were conducted by introducing a small-signal test source. The test source applied a small AC stimulus, and the resulting voltage and current were measured. The impedance was then calculated using the relationship:

$$Z = \frac{V}{I}$$

In the measurement, an AC signal with a magnitude of 1V was applied. With this setup, the impedance can be directly calculated as the reciprocal of the resulting current:

$$Z = \frac{1}{I}$$

$$R_{in,max} = 2.7[G\Omega]:$$

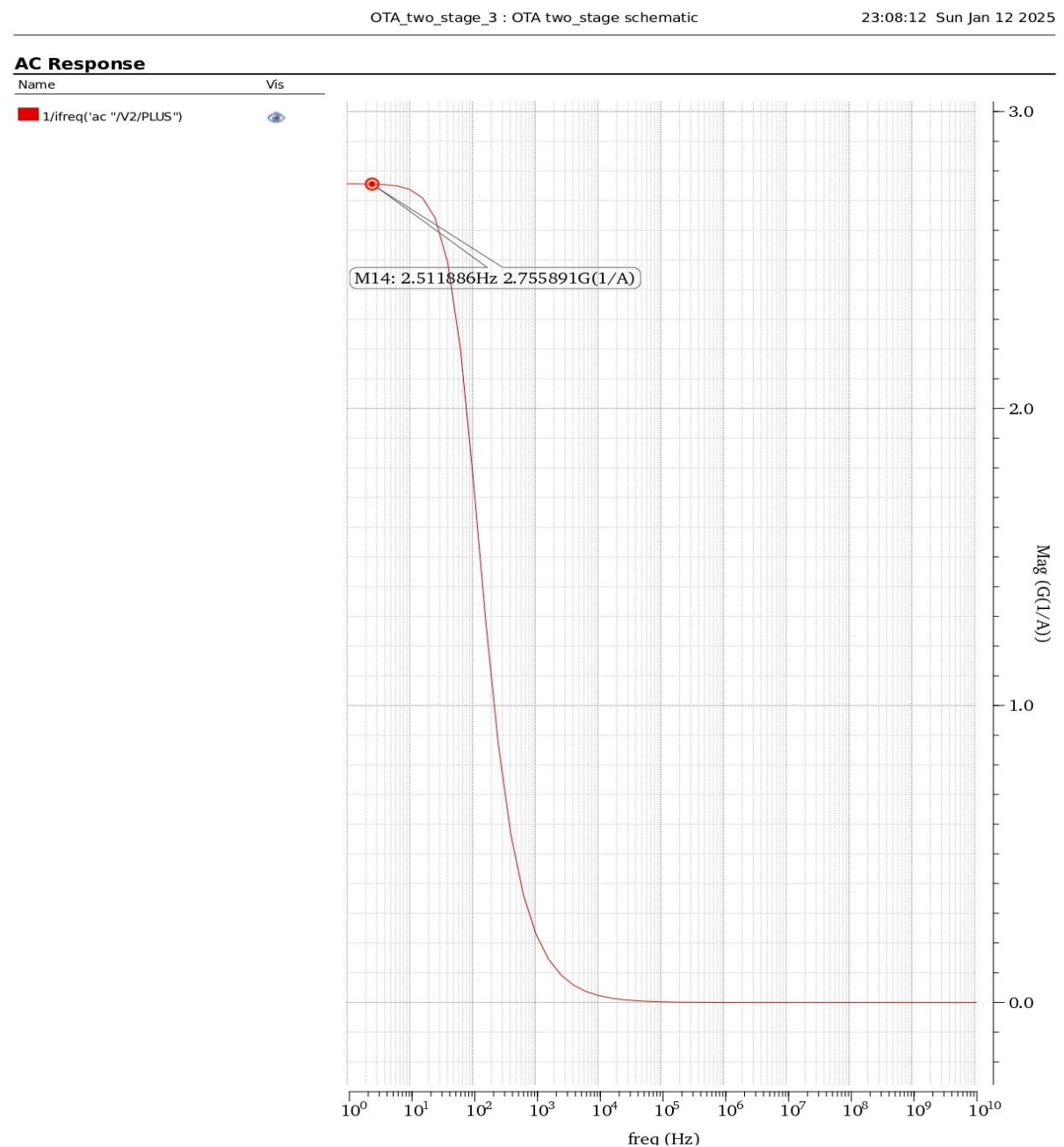



$$R_{out,max} = 3.9[k\Omega]:$$


Window 252

22:53:31 Sun Jan 12 2025

# 1/ifreq('ac "/V2/PLUS")

Name Vis

1/ifreq('ac "/V2/PLUS")

 

### Transient Simulation: Output Voltage Swing for a differential input signal of 0.5mV amplitude and 1kHz frequency


voltage swing shows the range the circuit's output can achieve without distortion or clipping. It reflects the amplifier's ability to reproduce the input signal.

From the simulation results we got a sine wave with:

- Maximum voltage:  $V_{max} = 598.0372 \text{ mV}$
- Minimum voltage:  $V_{min} = -503.5173 \text{ mV}$

the voltage swing is calculated as:
 
$$V_{pp} = 598.0372 \text{ mV} - (-503.5173 \text{ mV}) = 1101.5545 \text{ mV} \approx 1.1 \text{ V}$$




### Transient Simulation: Slew Rate


To evaluate the slew rate of the amplifier, a transient simulation was performed using an 1V impulse source as the input signal. The impulse signal ensures a rapid change at the input, driving the amplifier into a slew-limited region.

The slope of the steepest part of the output voltage was calculated to determine the slew rate:
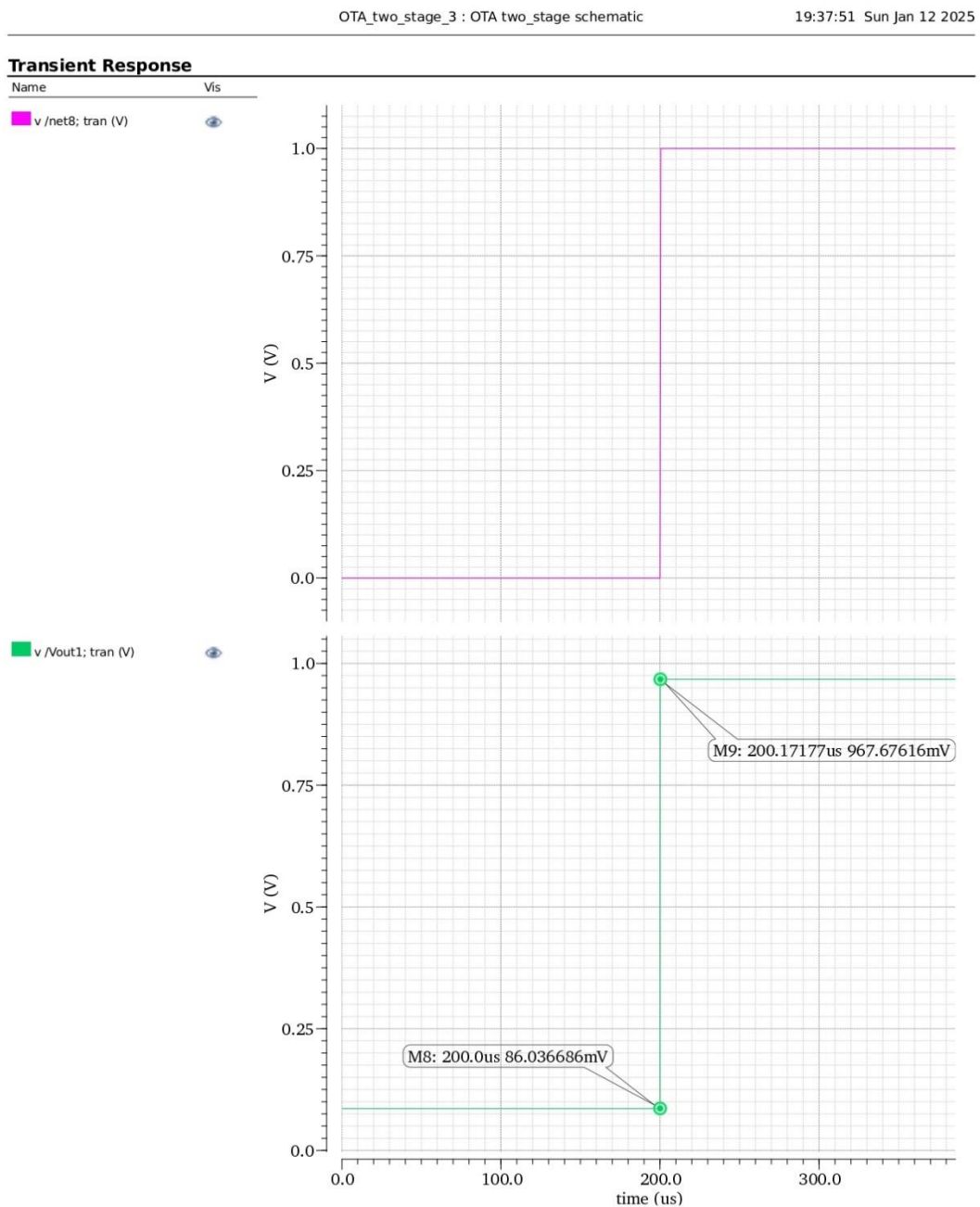
$$\text{Slew Rate} = \frac{\Delta V_{out}}{\Delta t} = \frac{967.67616\text{mV} - 86.036686\text{mV}}{200.17177\mu\text{s} - 200\mu\text{s}} = 5.13 \left[ \frac{\text{V}}{\mu\text{s}} \right]$$



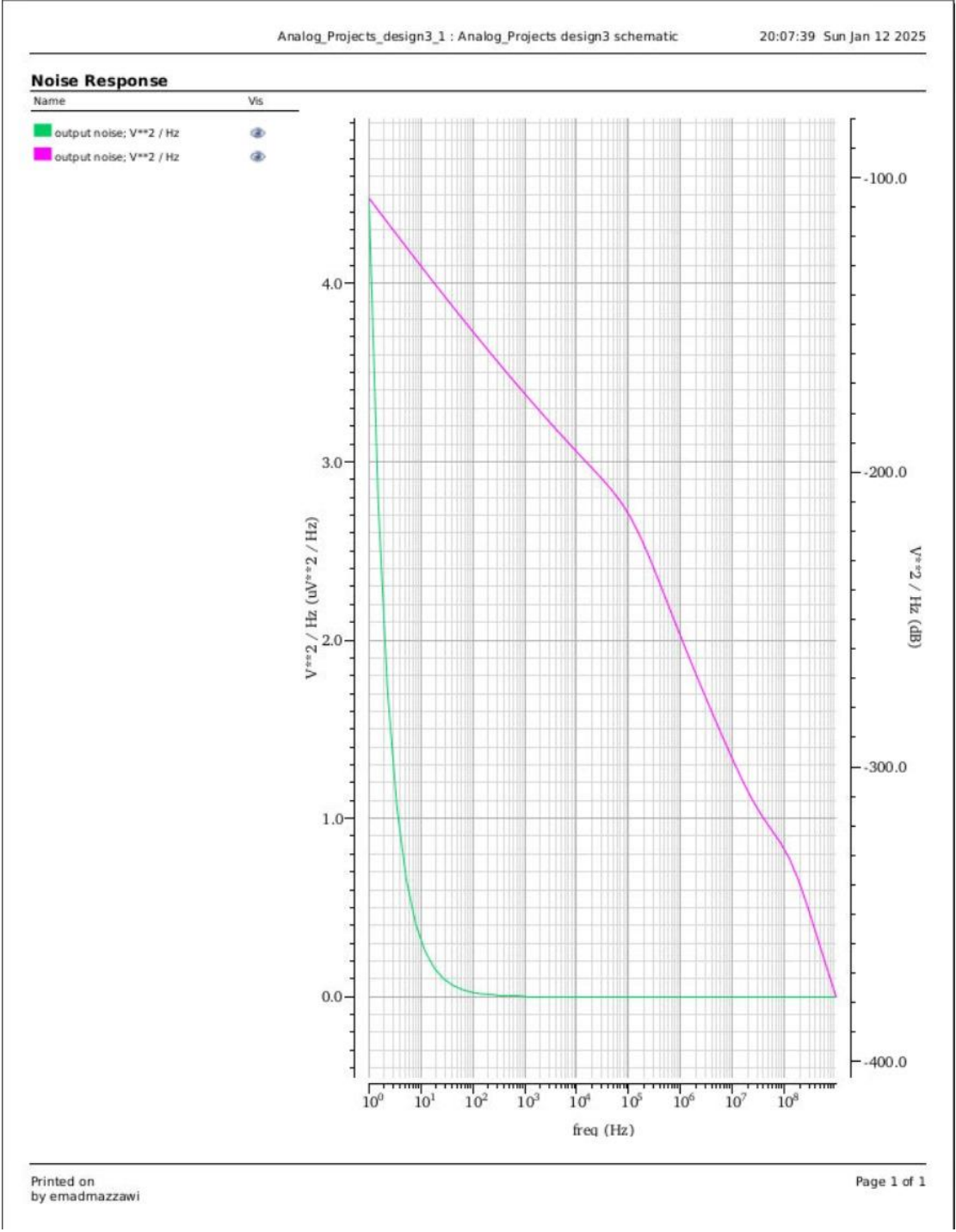Noise Simulation: Output Referred Voltage and Current Noise






**Noise Response**

Name Vis

input noise; V / sqrt(Hz)

 

## Noise Simulation: noise summary

The screenshot displays the Cadence Virtuoso interface with two windows open: 'Results Display Window' and 'Noise Summary'.

**Results Display Window (on micron3.eng.tau.ac.il)**

Device	Param	Noise Contribution	% Of Total
/M8	Rgatenoise	7.4366e-18	21.17
/M6	Sthd	4.64543e-18	13.23
/M5	Rgatenoise	4.17832e-18	11.90
/M6	Djnoise	3.43737e-18	9.79
/M8	Sthd	2.82045e-18	8.03
/M1	Sthd	2.2375e-18	6.37
/M2	Sthd	2.23122e-18	6.35
/M2	Rgatenoise	1.89976e-18	5.41
/M1	Rgatenoise	1.87151e-18	5.33
/M5	Sthd	1.26136e-18	3.59

Spot Noise Summary (in V<sup>2</sup>/Hz) at 100M Hz Sorted By Noise Contributors  
Total Summarized Noise = 3.51198e-17  
Total Input Referred Noise = 8.74281e-17  
The above noise summary info is for noise data

**Noise Summary (on micron3.eng.tau.ac.il)**

Print the output noise of 'noise' analysis

Type: ☒ spot noise ☐ integrated noise noise unit: V<sup>2</sup>

Frequency Spot (Hz): 100M

FILTER

hierarchy level: ☒

Include All Types: ☐ Include None: ☐

Include instances:  Select Clear

Exclude instances:  Select Clear

TRUNCATE & SORT

truncate: by number top 10

sort by: ☒ noise contributors ☐ composite noise ☐ device name

OPTIONS

Consolidate iterated instances: ☐ Suffix notation: ☐

Write RCNet: ☐


Buttons: OK Cancel Apply Help


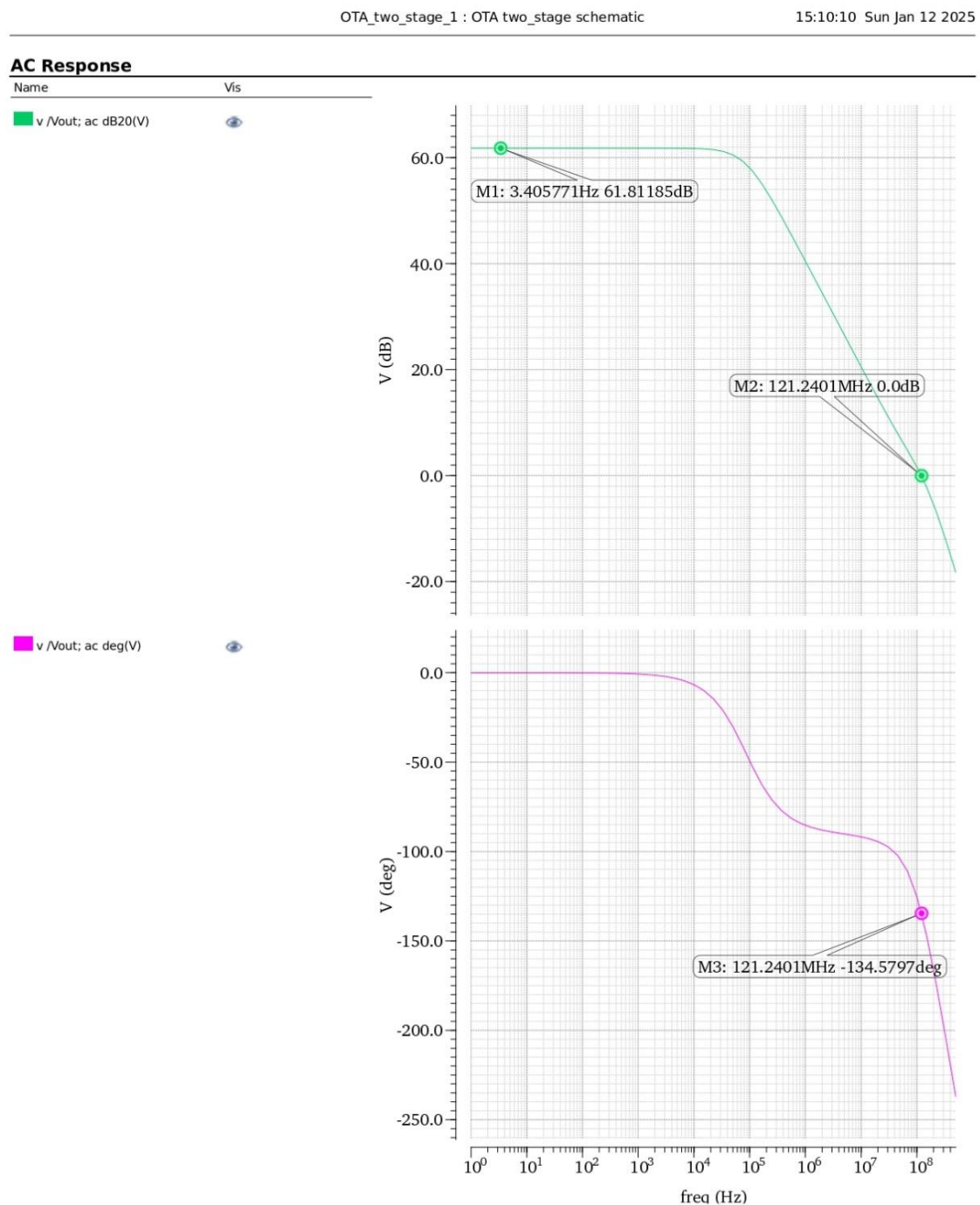
## Stability Simulation

After adding the compensation loop, the stability of the two-stage OTA was analyzed. The compensation network ensures a sufficient phase margin by introducing a dominant pole, enabling reliable closed-loop operation. The following simulation illustrates the stability improvements achieved:

The results show that the amplifier attains a low-frequency gain of **61.8 dB**, a gain-bandwidth product of **121.24 MHz**, and demonstrates the anticipated change in the phase response to give us a more stable OTA:



Performing stability measurements will provide the following stability parameters:

Stability Summary - circuit "two_stage" with loop probe "IPRB0"			
PM(deg)	@Freq(Hz)	GM(dB)	@Freq(Hz)
113.44	79.9M	2.763	605.17M

And our amplifier is stable enough.

### Summery

Parameter	Required Value	Design Achieved Value	Physical
Minimum small signal Gain - $A_0$	60	61.8	<i>dB</i>
Minimum GBW	100	121.24	<i>MHz</i>
Phase Margin	>45	113.44	<i>Degrees</i>
Power Dissipation	Keep as low as possible	6.063	<i>mW</i>